

ENR-325/325L Principles of Digital Electronics and Laboratory

Xiang Li
Fall 2025

Hamming codes can be done in the EE way

- Before that, we need to acquire some basic skillsets.

Pre-step: Data forms

Step 1: Data manipulation

Step 2: Information storage


Step 3: Interface

3.1 Information flow

~~3.2 Physical contacts~~ (better stuff to talk about in PCB designs)

Understanding SR latch with truth table and timing diagram


SR latch

 


SR latch truth table

S	R	Output (Q)
0	0	Previous State (HOLD)
0	1	0
1	0	1
1	1	0 (Invalid)

SR Latch Timing Diagram (NOR Gates)

 


A latch with a “single” input

 

[https://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](https://en.wikipedia.org/wiki/Flip-flop_(electronics))

A gated D latch

 


D latch truth table


D	E	Output (Q)
X	0	Previous State
0	1	0
1	1	1

A latch with a “single” input


A gated D latch

 




Also known as: D latch/data latch

 


Gated D latch

 


A clocked D latch

   


Timing diagram code:

 
 
```
1 {  
2   "signal": [  
3     {"name": "CLK",      "wave": "lhlhlhl"},  
4     {"name": "D",        "wave": "lpphppl"},  
5     {"name": "Q",        "wave": "lp lh.pl"},  
6   ],  
7   "head": {  
8     "text": "Clocked gated D latch)"  
9   },  
10  "config": {  
11    "hscale": 2  
12  }  
13 }  
14 }  
15 }  
16 }
```




 Rising edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:
Master-slave D type flip flop

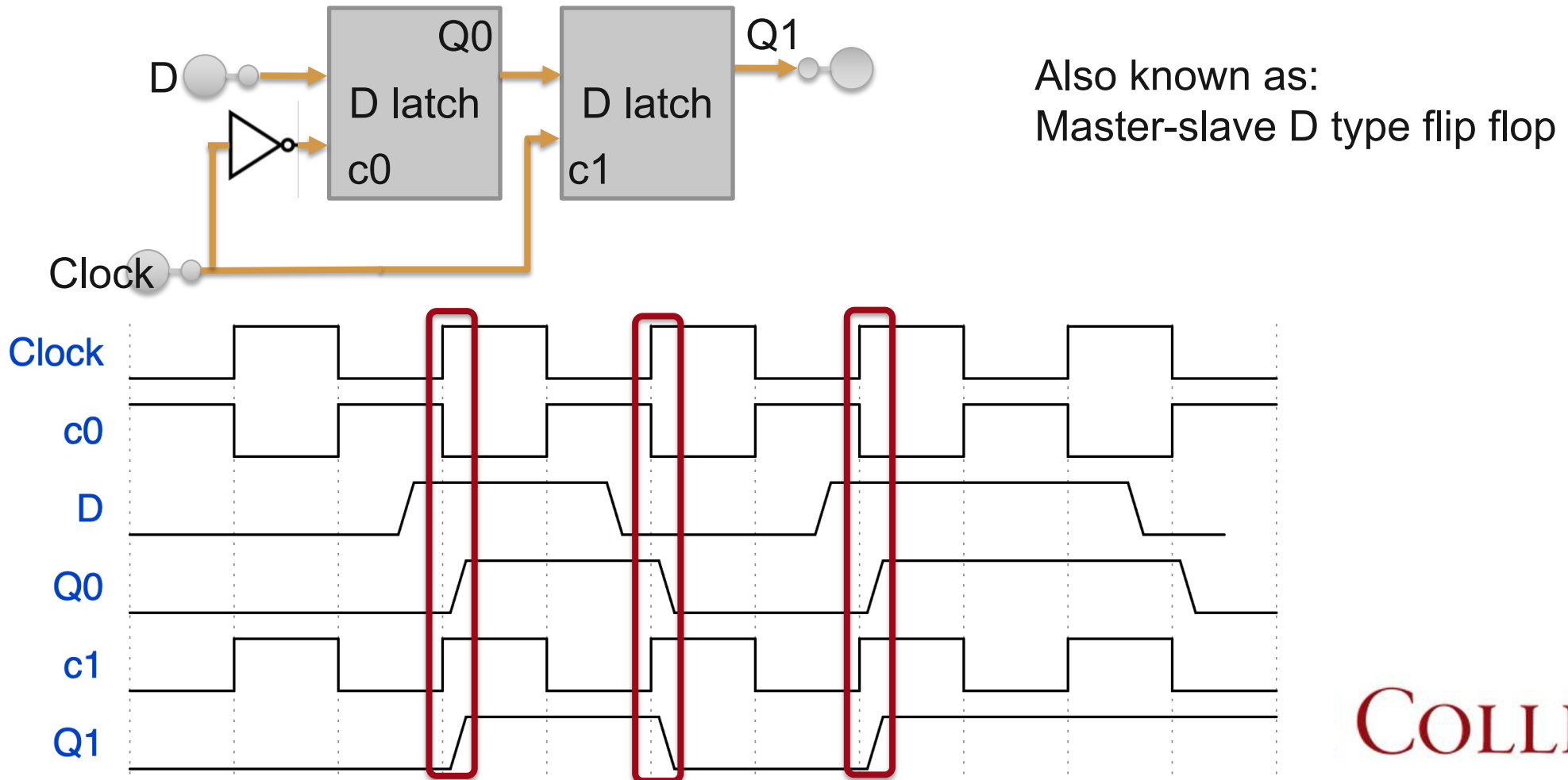Rising edge-triggered flip flops: synchronizing (timed trigger) achieved



 
Falling edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:
Master-slave D type flip flop

Timing diagram is in HW#7.


One more application with D flip-flops

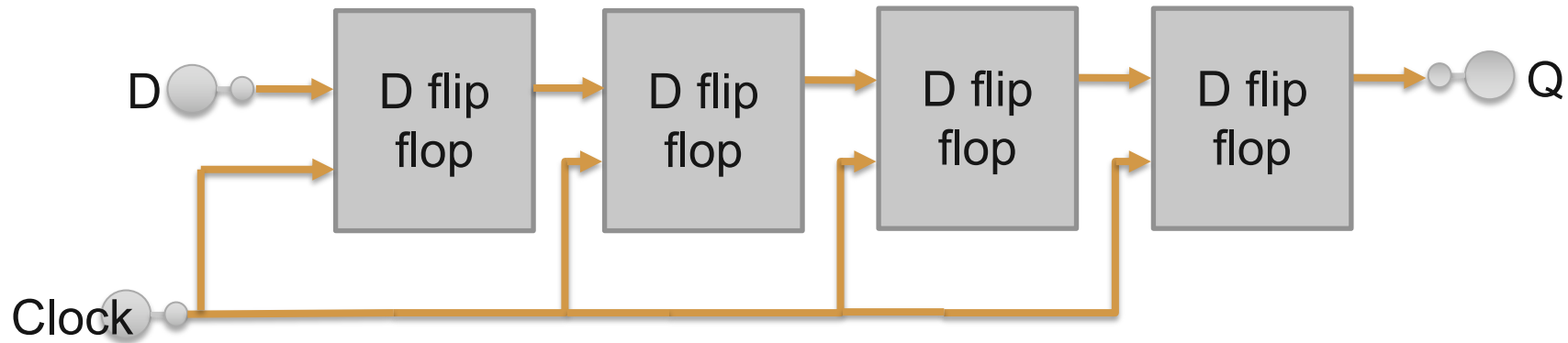

So, this is a (4 bit) shift register

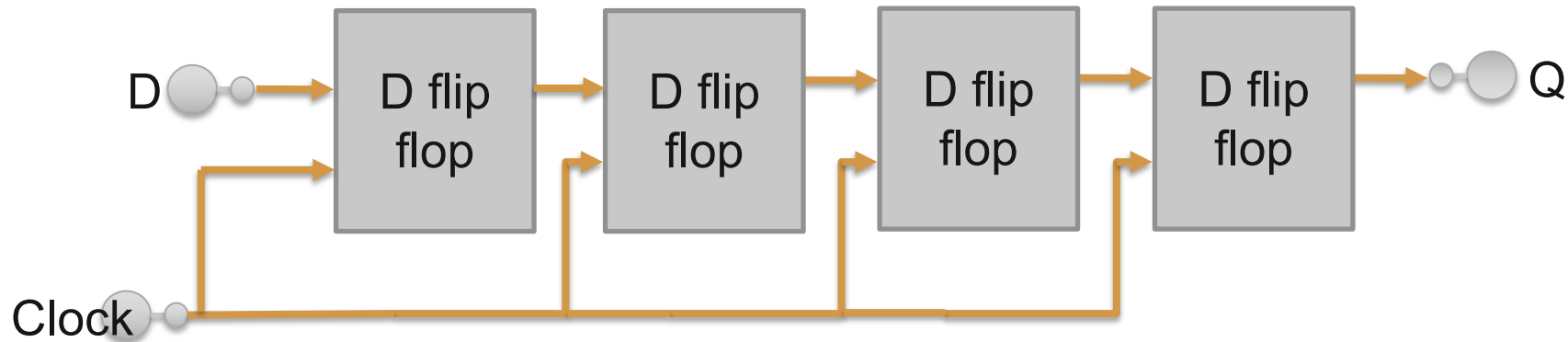


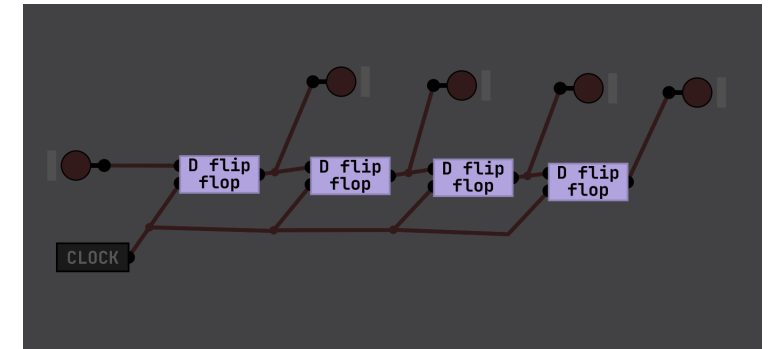- **Serial In (SI), Serial Out (SO)**
- **How about SIPO, PISO, and PIPO?**



Dynamic discipline: handling the interface between logics and time

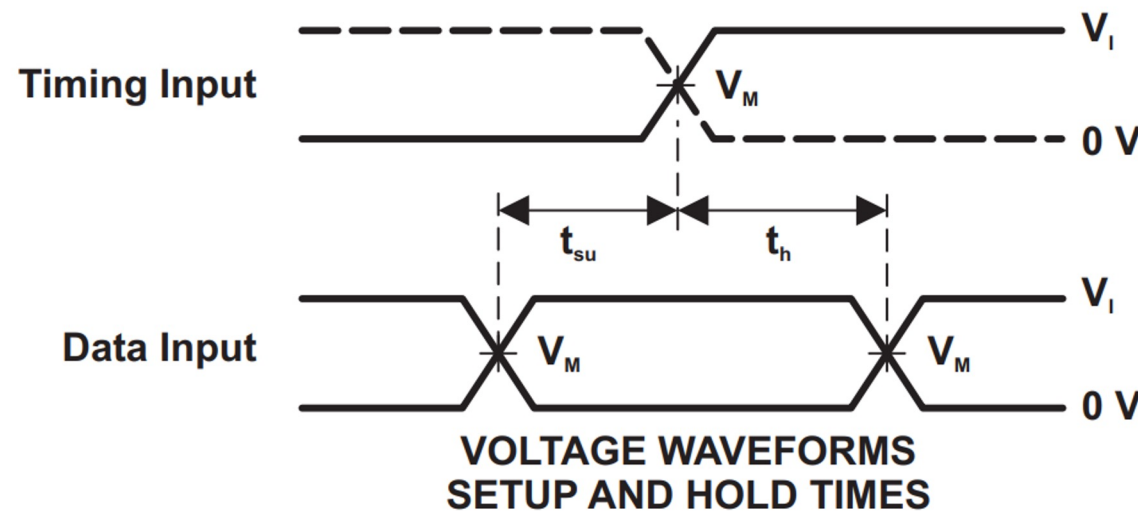- A clock signal (with its edges if it's a flip-flop) to define transitions.
- Stable inputs during that transition window. (So, some *setup time* t_{su} and some *hold time* t_h)
- Thus, guaranteed viable output other than its own switching delays.






COE COLLEGE®

Dynamic discipline: handling the interface between logics and time

- Unlike propagation delay (t_{pd}) and contamination delay (t_{cd}), the setup time t_{su} and hold time t_h are intentional.
- So, the final time constraint for sequential logics is:

Minimum clock period: $T_c \geq \Sigma t_{pd} + t_{su}$

   Minimum delay constraint: $\Sigma t_{cd} \geq t_h$



COE COLLEGE®

Dynamic discipline:


Timing Requirements (Over Recommended Operating Free-air Temperature Range (unless otherwise noted)) (see Figure 2)

			SN54LVTH16646				SN74LVTH16646				UNIT
			$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		
			MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
f_{clock}	Clock frequency		150		150		150		150		MHz
t_w	Pulse duration, CLK high or low		3.3		3.3		3.3		3.3		ns
t_{su}	Setup time, A or B before CLKAB↑ or CLKBA↑	Data high	1.2		1.5		1.2		1.5		ns
		Data low	2		2.8		2		2.8		
t_h	Hold time, A or B after CLKAB↑ or CLKBA↑	Data high	0.5		0		0.5		0		ns
		Data low	0.5		0.5		0.5		0.5		


Figure 14. Example Timing-Requirements Section

MUX:

Typical symbol you'll see

 


Typical switching schematic you'll see

 

Typical logic schematic you'll see

2-input Multiplexer Design

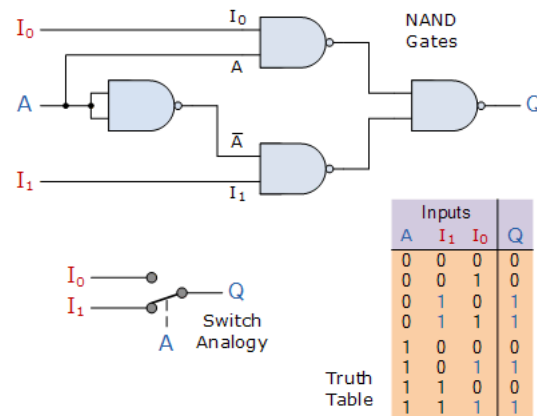

Same truth table?

A	I_1	I_2	Q
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

Same truth table?

A	Q
0	I_1
1	I_2



COE COLLEGE

MUX IRL:




TMUX5411, TMUX5412, TMUX5413
SCDS485A – JULY 2025 – REVISED SEPTEMBER 2025

TMUX541x 50V, 21Ω, 1:1 (SPST) 4-Channel Switches with 1.8V Logic

No logic schematics?

7.2 Functional Block Diagram

 

7.4.1 Truth Tables

TMUX5412 Truth Table provides the truth table for TMUX541x.

Table 7-1. TMUX5411 Truth Table

SEL x ⁽¹⁾	CHANNEL x
0	Channel x ON
1	Channel x OFF

Table 7-2. TMUX5412 Truth Table

SEL x ⁽¹⁾	CHANNEL x
0	Channel x OFF
1	Channel x ON

Table 7-3. TMUX5413 Truth Table

SEL1	SEL2	SEL3	SEL4	ON / OFF CHANNELS ⁽¹⁾
0	X	X	X	CHANNEL 1 OFF
1	X	X	X	CHANNEL 1 ON
X	0	X	X	CHANNEL 2 ON
X	1	X	X	CHANNEL 2 OFF
X	X	0	X	CHANNEL 3 ON
X	X	1	X	CHANNEL 3 OFF
X	X	X	0	CHANNEL 4 OFF
X	X	X	1	CHANNEL 4 ON

(1) x denotes 1, 2, 3, or 4 for the corresponding channel.