

ENR-325/325L Principles of Digital Electronics and Laboratory

Xiang Li
Fall 2025

Hamming codes can be done in the EE way

- Before that, we need to acquire some basic skillsets.

Pre-step: Data forms

Step 1: Data manipulation

Step 2: Information storage


Step 3: Interface

3.1 Information flow

~~3.2 Physical contacts~~ (better stuff to talk about in PCB designs)

Understanding SR latch with truth table and timing diagram


SR latch

 


SR latch truth table

S	R	Output (Q)
0	0	Previous State (HOLD)
0	1	0
1	0	1
1	1	0 (Invalid)

SR Latch Timing Diagram (NOR Gates)

 


A latch with a “single” input

 

[https://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](https://en.wikipedia.org/wiki/Flip-flop_(electronics))

A gated D latch

 


D latch truth table


D	E	Output (Q)
X	0	Previous State
0	1	0
1	1	1

A latch with a “single” input


A gated D latch

 




Also known as: D latch/data latch

 


Gated D latch

 


A clocked D latch

   


Timing diagram code:

 
 
```
1 {  
2   "signal": [  
3     {"name": "CLK",      "wave": "lhlhlhl"},  
4     {"name": "D",        "wave": "lpphppl"},  
5     {"name": "Q",        "wave": "lp lh.pl"},  
6   ],  
7   "head": {  
8     "text": "Clocked gated D latch)"  
9   },  
10  "config": {  
11    "hscale": 2  
12  }  
13 }  
14 }  
15 }  
16 }
```




 Rising edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:
Master-slave D type flip flop

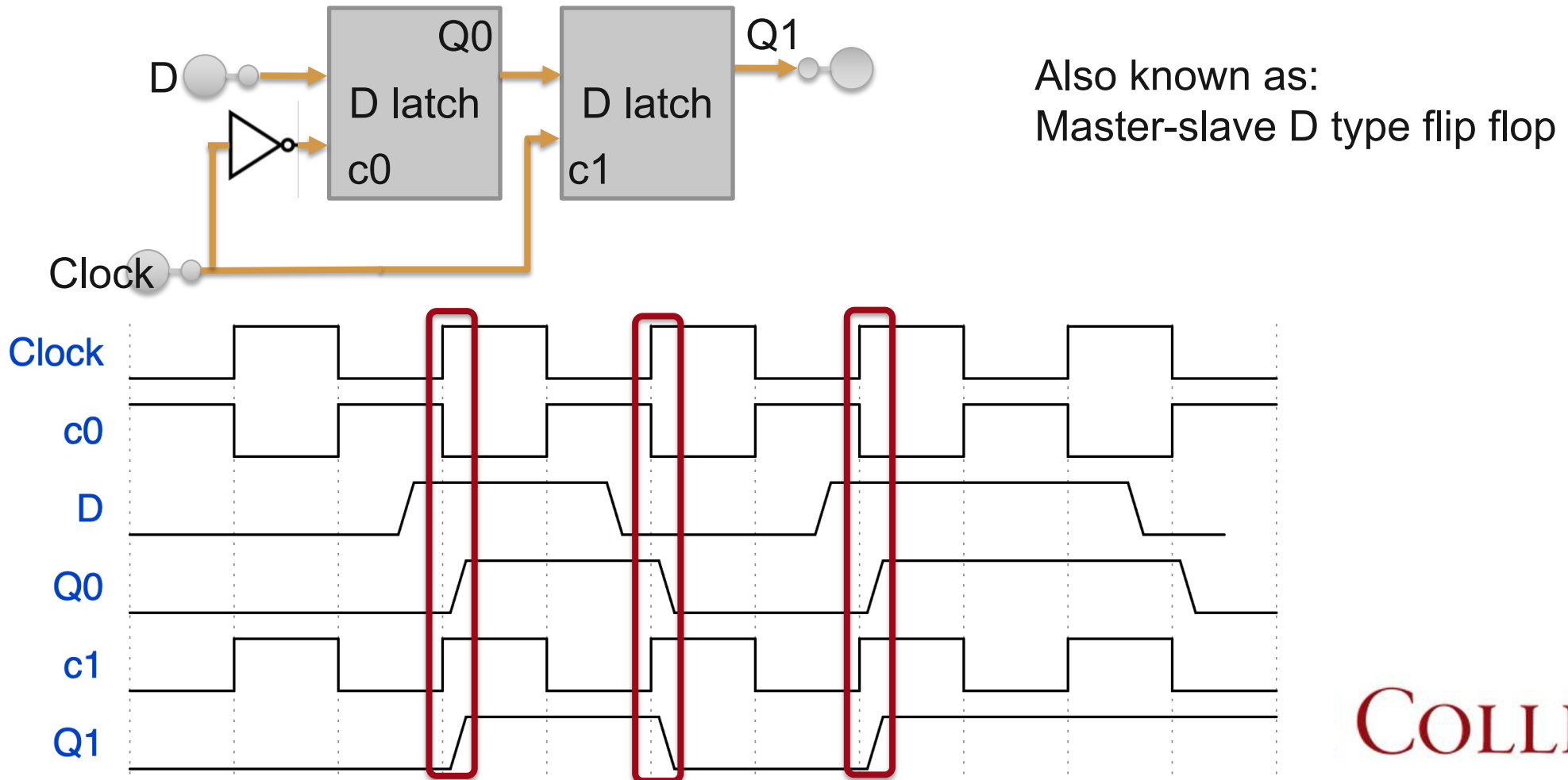Rising edge-triggered flip flops: synchronizing (timed trigger) achieved



 
Falling edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:
Master-slave D type flip flop

Timing diagram is in HW#7.


One more application with D flip-flops

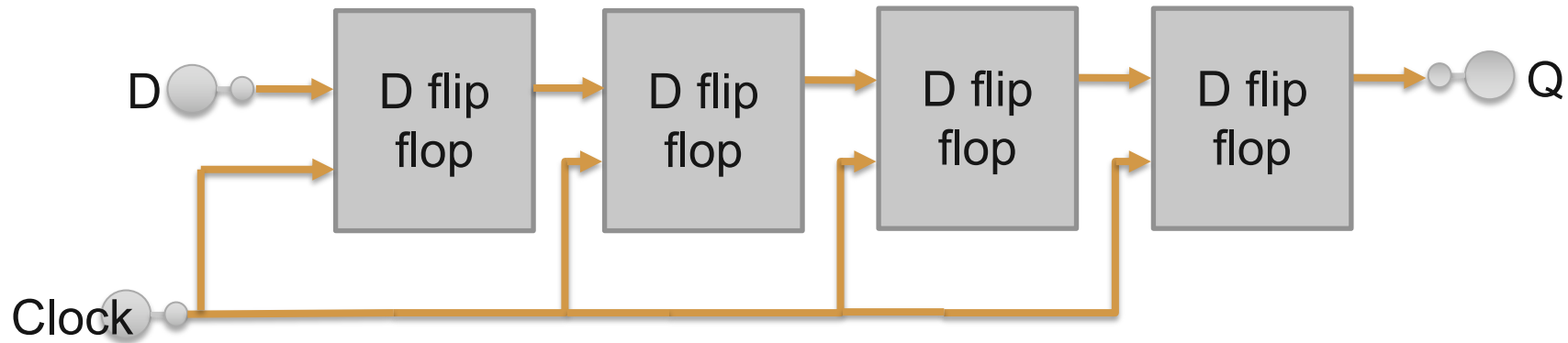

So, this is a (4 bit) shift register

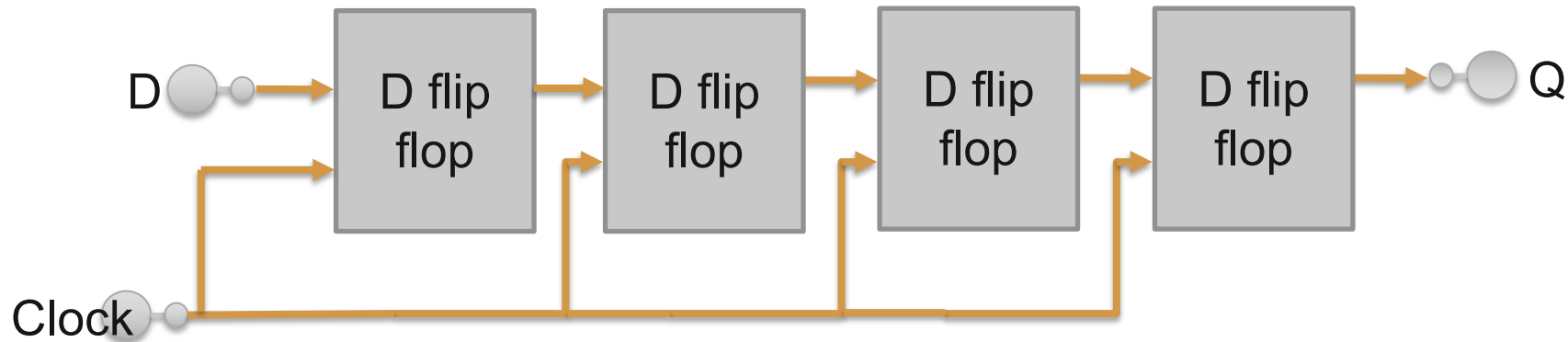


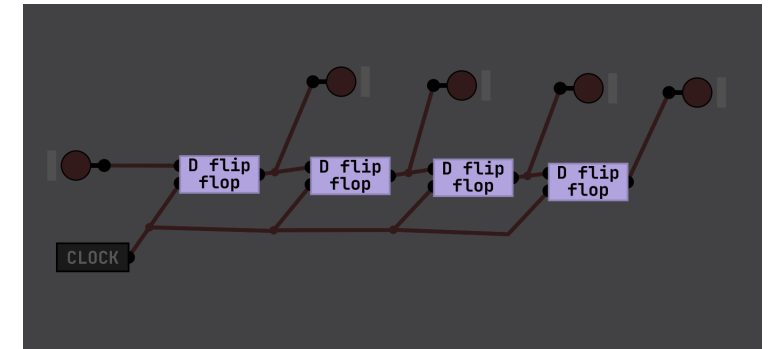- **Serial In (SI), Serial Out (SO)**
- **How about SIPO, PISO, and PIPO?**



Dynamic discipline: handling the interface between logics and time

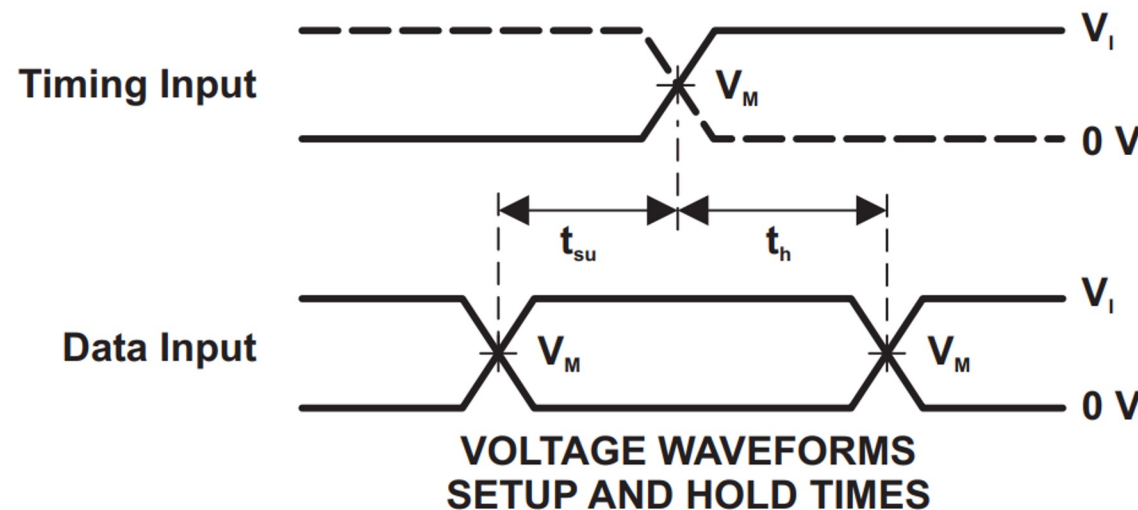- A clock signal (with its edges if it's a flip-flop) to define transitions.
- Stable inputs during that transition window. (So, some *setup time* t_{su} and some *hold time* t_h)
- Thus, guaranteed viable output other than its own switching delays.






COE COLLEGE®

Dynamic discipline: handling the interface between logics and time

- Unlike propagation delay (t_{pd}) and contamination delay (t_{cd}), the setup time t_{su} and hold time t_h are intentional.
- So, the final time constraint for sequential logics is:

Minimum clock period: $T_c \geq \Sigma t_{pd} + t_{su}$

   Minimum delay constraint: $\Sigma t_{cd} \geq t_h$



COE COLLEGE®

Dynamic discipline:


Timing Requirements (Over Recommended Operating Free-air Temperature Range (unless otherwise noted)) (see Figure 2)

			SN54LVTH16646				SN74LVTH16646				UNIT
			$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		
			MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
f_{clock}	Clock frequency		150		150		150		150		MHz
t_w	Pulse duration, CLK high or low		3.3		3.3		3.3		3.3		ns
t_{su}	Setup time, A or B before CLKAB↑ or CLKBA↑	Data high	1.2		1.5		1.2		1.5		ns
		Data low	2		2.8		2		2.8		
t_h	Hold time, A or B after CLKAB↑ or CLKBA↑	Data high	0.5		0		0.5		0		ns
		Data low	0.5		0.5		0.5		0.5		


Figure 14. Example Timing-Requirements Section

Multiplexer (MUX):

Typical symbol you'll see

 


Typical switching schematic you'll see

 

Typical logic schematic you'll see

2-input Multiplexer Design

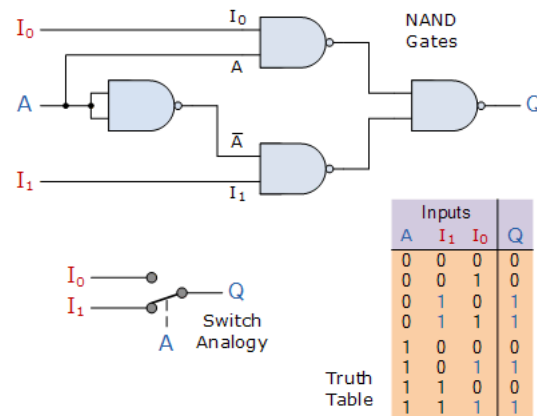

Same truth table?

A	I_1	I_2	Q
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

Same truth table?

A	Q
0	I_1
1	I_2



COE COLLEGE

MUX IRL:




TMUX5411, TMUX5412, TMUX5413
SCDS485A – JULY 2025 – REVISED SEPTEMBER 2025

TMUX541x 50V, 21Ω, 1:1 (SPST) 4-Channel Switches with 1.8V Logic

- No logic schematics?
- When to use MUX?

7.2 Functional Block Diagram

 

7.4.1 Truth Tables

TMUX5412 Truth Table provides the truth table for TMUX541x.

Table 7-1. TMUX5411 Truth Table

SEL x ⁽¹⁾	CHANNEL x
0	Channel x ON
1	Channel x OFF

Table 7-2. TMUX5412 Truth Table

SEL x ⁽¹⁾	CHANNEL x
0	Channel x OFF
1	Channel x ON

Table 7-3. TMUX5413 Truth Table

SEL1	SEL2	SEL3	SEL4	ON / OFF CHANNELS ⁽¹⁾
0	X	X	X	CHANNEL 1 OFF
1	X	X	X	CHANNEL 1 ON
X	0	X	X	CHANNEL 2 ON
X	1	X	X	CHANNEL 2 OFF
X	X	0	X	CHANNEL 3 ON
X	X	1	X	CHANNEL 3 OFF
X	X	X	0	CHANNEL 4 OFF
X	X	X	1	CHANNEL 4 ON

(1) x denotes 1, 2, 3, or 4 for the corresponding channel.

The last piece of interface: the flow of data

The plan is to cover: I²C, SPI, and UART

I²C: Inter-integrated circuit protocol

(Born in 1982)

A Basic Guide to I²C



Joseph Wu

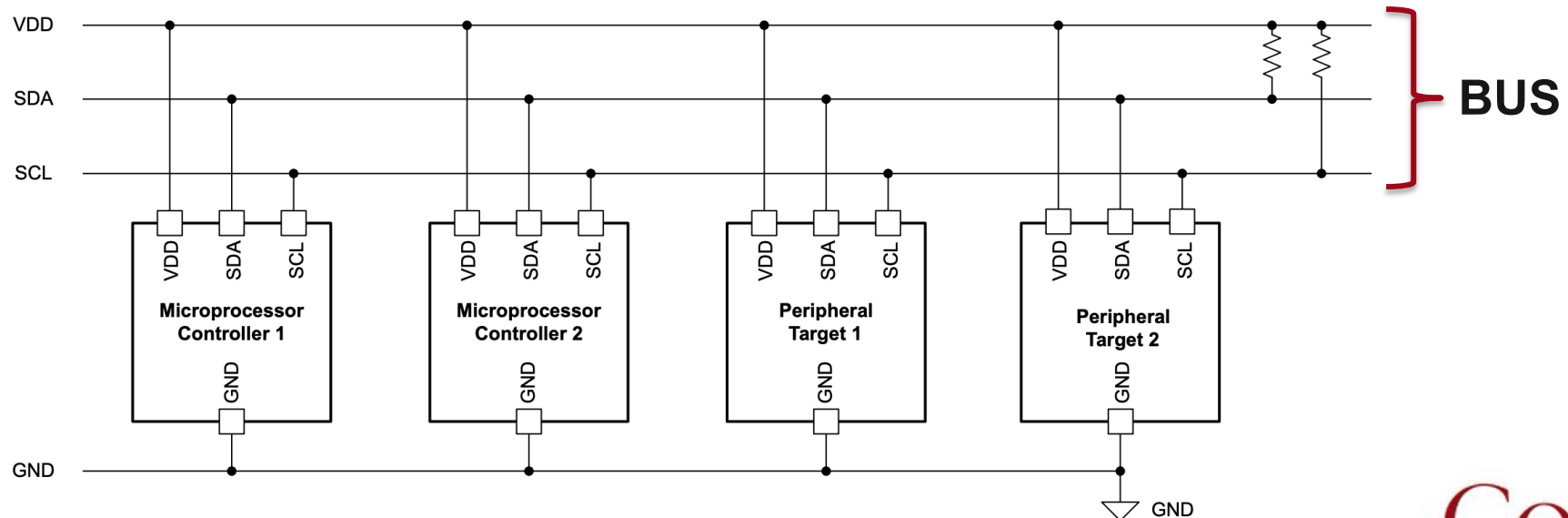


Figure 2-1. Typical I²C Implementation

I²C: how signaling works (open-drain)



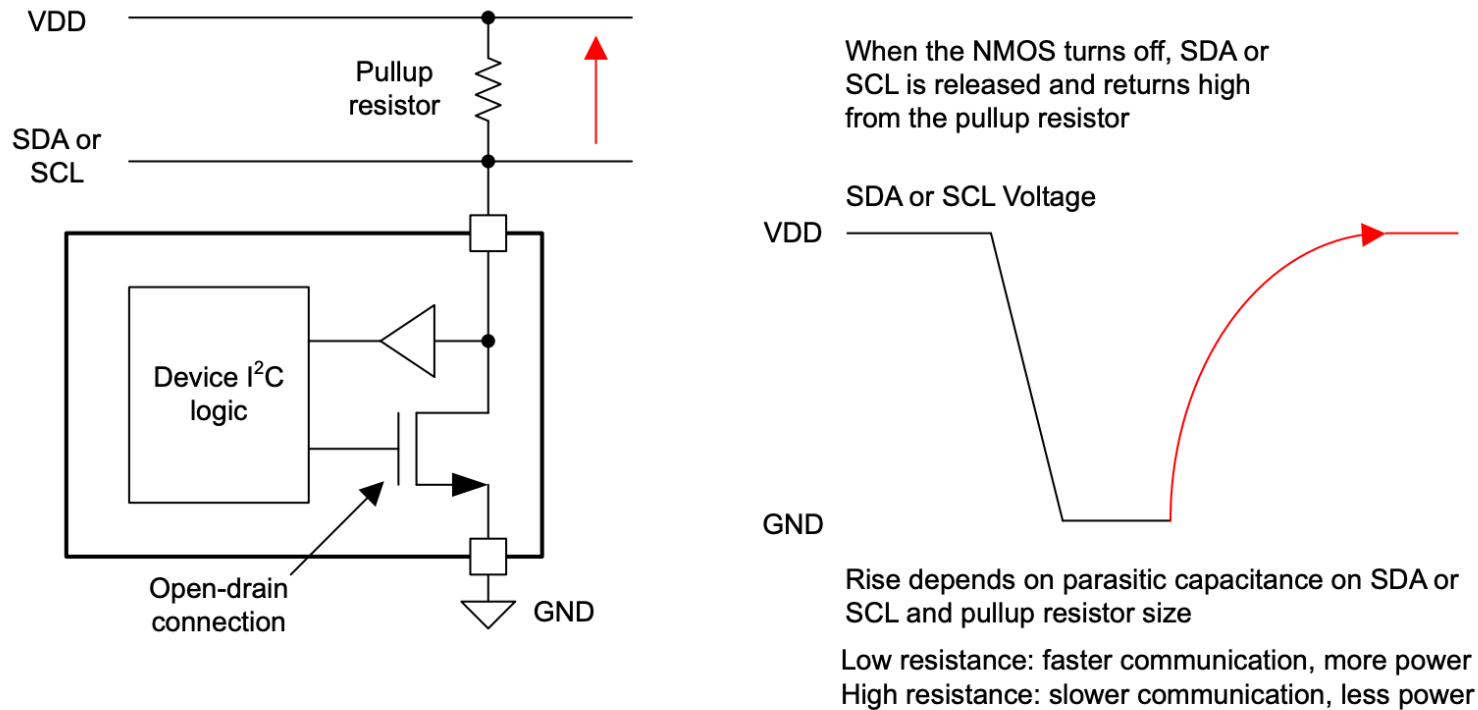


Figure 2-3. Pullup Resistor Pulls Line High When NMOS is Turned Off

I²C: how signaling works

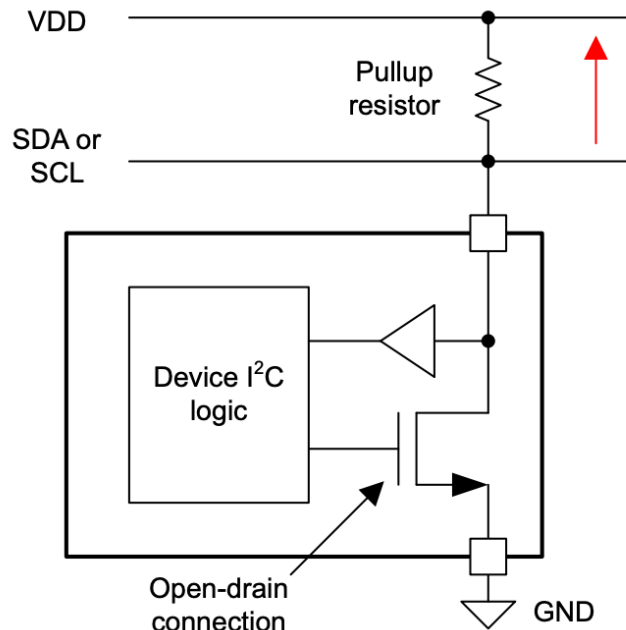

 When the NMOS turns off, SDA or SCL is released and returns high from the pullup resistor



Rise depends on parasitic capacitance on SDA or SCL and pullup resistor size

Low resistance: faster communication, more power
High resistance: slower communication, less power

 


Figure 2-3. Pullup Resistor Pulls Line High When NMOS is Turned Off

Potential issue for multiple I²C on the line?

I²C: data frames

How to start and stop:

 


Figure 3-1. I²C START and STOP

How to tell high and low:

 


Figure 3-2. I²C Digital One and Zero Representations

I²C: data frames

How to pick who to read and write:


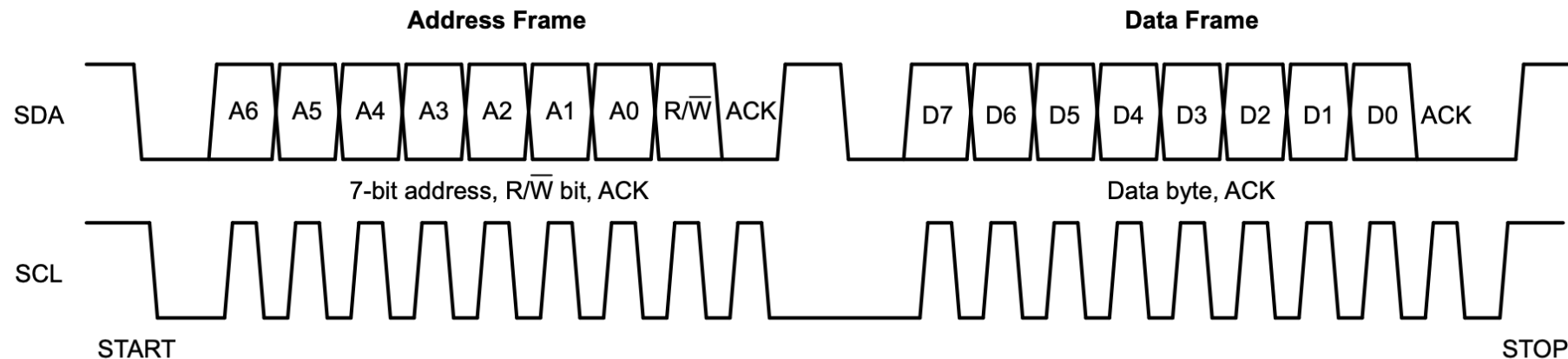


Figure 3-3. I²C Address and Data Frames

- 7-bit address, but some address are reserved.
- R (read): 1
W (write): 0
- ACK (acknowledge): 0
NACK (no ACK): 1

I²C in works:

Step 1: who to talk (address frame)

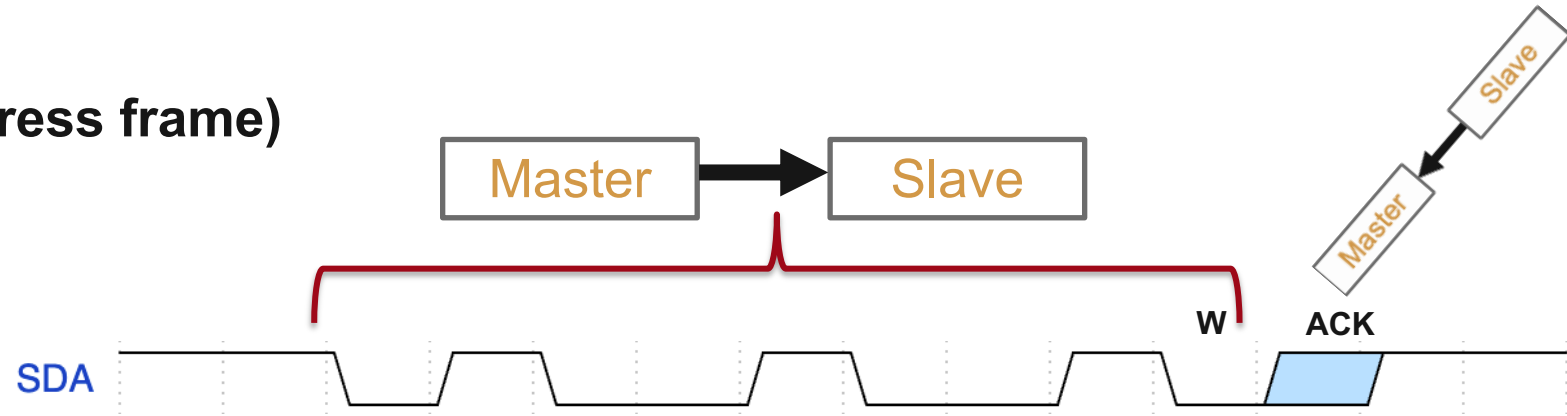

Step 2: what to talk (data frame)

