

ENR-325/325L Principles of Digital Electronics and Laboratory

Xiang Li
Fall 2025


Configuration on the go: PLD and FPGA

- PLD: Programmable Logic Device
 - ▶ PROM: Programmable Read-Only Memory (1960s)
 - ▶ PLA: Programmable Logic Array (1970s)
 - ▶ PAL: Programmable Array Logic (1970s)
- FPGA: Field-Programmable Gate Array (1990s)

What is the meaning of hardware coding?

As a small dev:

 There's NO IC design. This is the only standard CMOS layout I can afford.
(2 input, 2 output, four D flip-flops).




What is the meaning of hardware coding?


But the top wiring (aka additional routing layer) is another story.

This is GA (Gate-Arrays).

 The cost is greatly reduced since I only need to pay for the customized top layer.



This is a two 2-bit data I/O.


 


This is a one 4-bit data I/O.

What is the meaning of hardware coding?


And if there are built-in wiring on the IC level, we can greatly increase the speed of the chip.

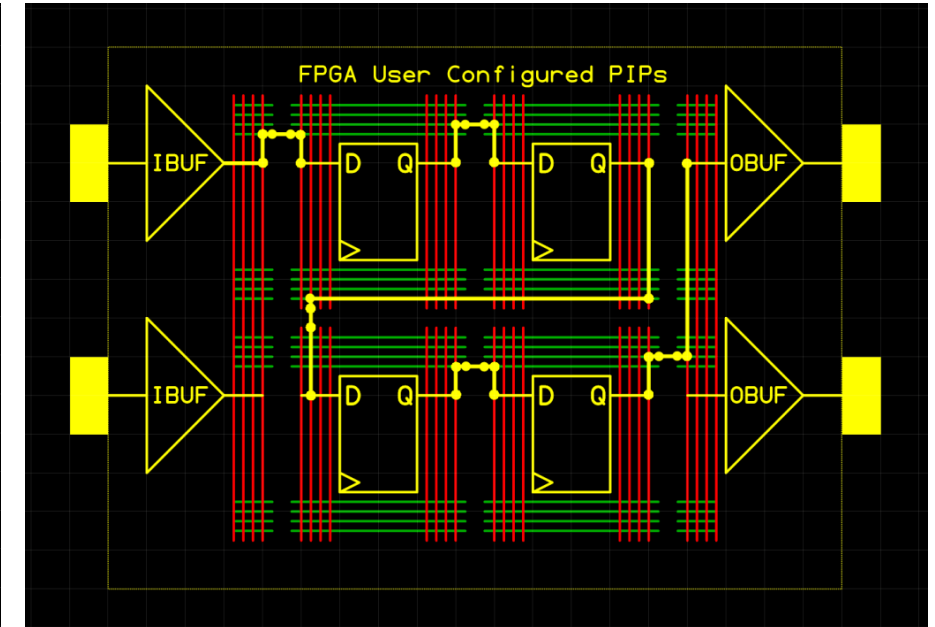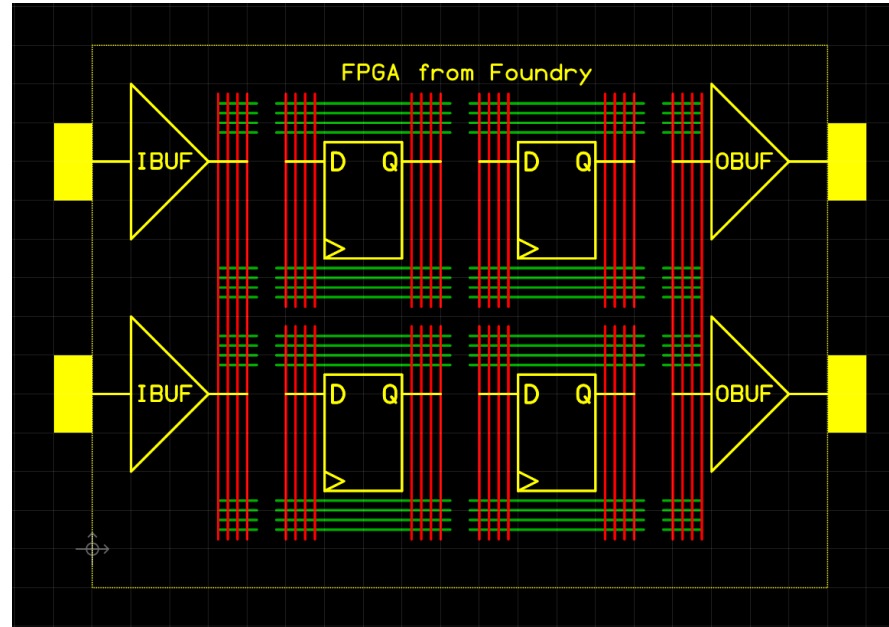The build-in wiring is called: **Programmable Interconnect Points (PIPs)**.



How PIPs are done in the early days:

Do less by doing more:

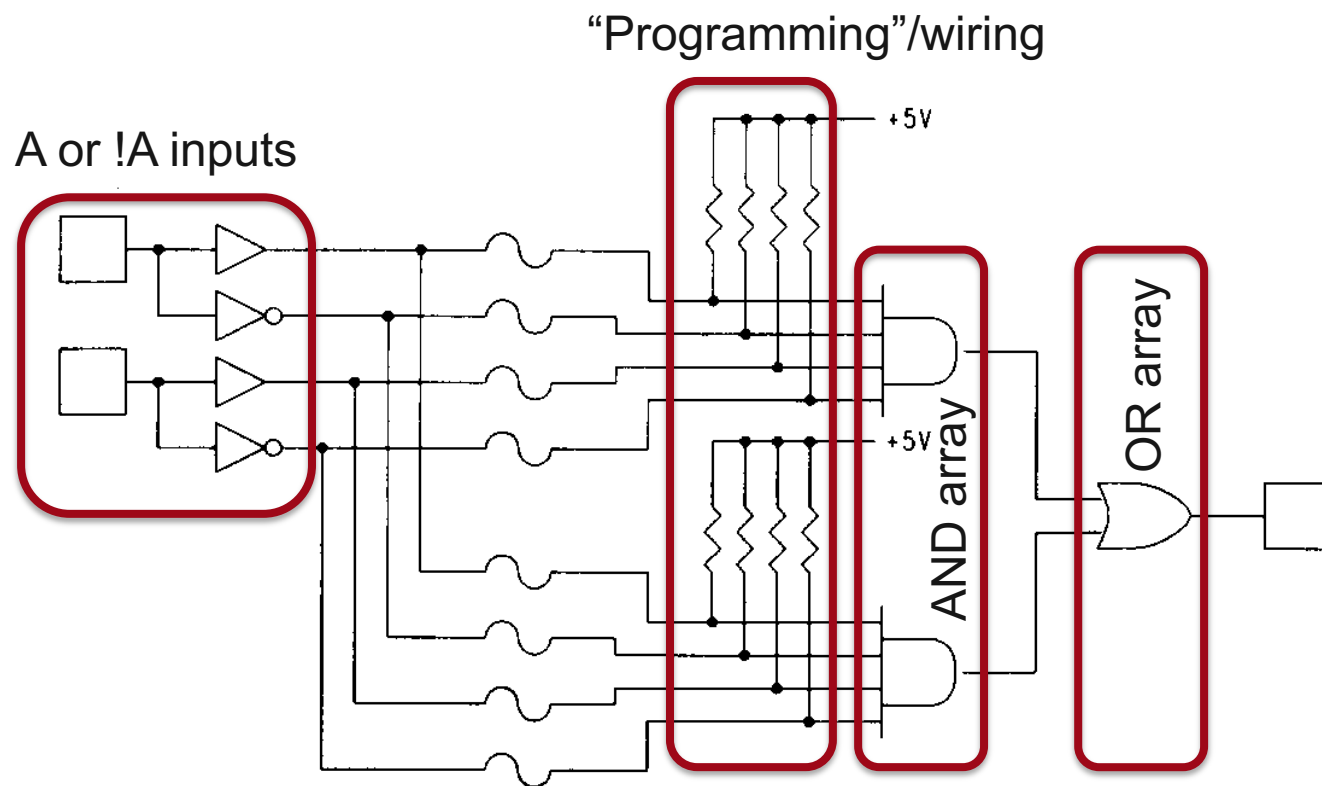


Example of codes (1989) that do the wiring:

```
ABEL(tm) 3.20 Data I/O Corp. JEDEC file for: P16R4 V8.0
4 bit counter with synchronous clear
Michael Holley and Dave Pellerin*
QP20* QP2048* QV6* F0*
NOTE Table of pin names and numbers*
NOTE PINS Q3:14 Q2:15 Q1:16 Q0:17 Clk:1 Clear:2 OE:11*
L0512 01111111111111111111111111111111*
L0544 11111111101111111111111111111111*
L0768 01111111111111111111111111111111*
L0800 11111111101110111111111111111111*
L0832 11111111110111011111111111111111*
L1024 01111111111111111111111111111111*
L1056 11111111101110111011111111111111*
L1088 11111111110111111101111111111111*
L1120 11111111111111011101111111111111*
L1280 01111111111111111111111111111111*
L1312 11111111101110111011101111111111*
L1344 11111111110111111111111110111111*
L1376 11111111111110111111110111111111*
L1408 11111111111111111111101110111111*
V0001 C1XXXXXXXXX0XKLLLLXKN*
V0002 C0XXXXXXXXX0XKLLHLXKN*
V0003 C0XXXXXXXXX0XKLLHLXKN*
V0004 C0XXXXXXXXX0XKLLHLXKN*
V0005 C0XXXXXXXXX0XKLLHLXKN*
V0006 C1XXXXXXXXX0XKLLLLXKN*
C337C*
```



COE COLLEGE


Let's do higher level of abstraction:

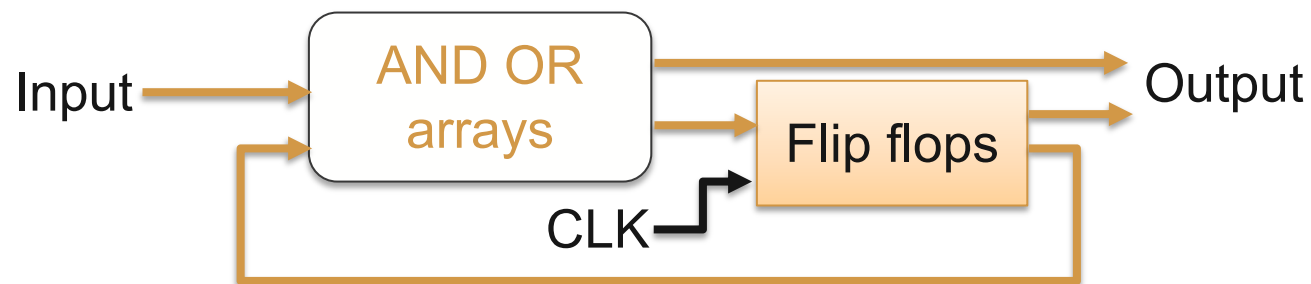

With the help of flip flops, now the system can store **state** variables.
The system can then output:

- Function of states (Moore machine)
- Function of states and inputs (Mealy machine)


Let's do higher level of abstraction:

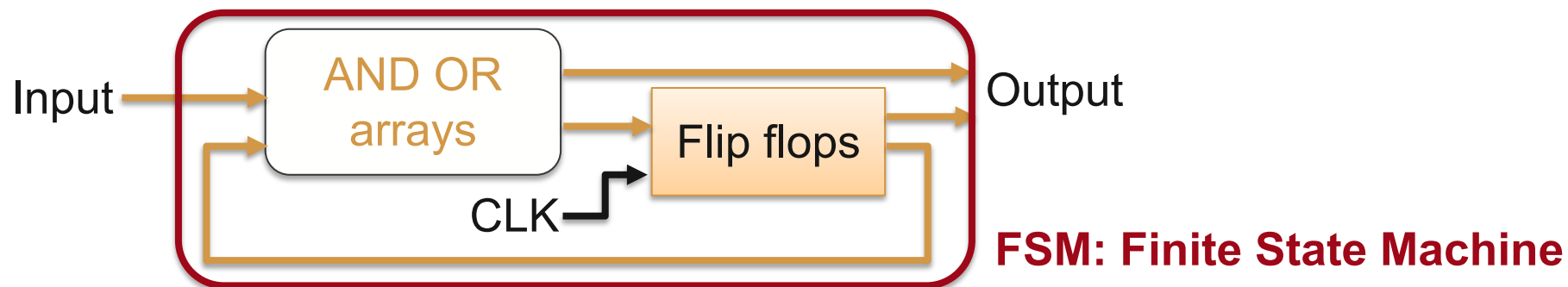


With the help of flip flops, now the system can store **state** variables.
The system can then output:

- Function of states (Moore machine)
- Function of states and inputs (Mealy machine)

 Let's do even a higher level of abstraction:



Complex Programmable Logic Device - CPLD

 

Programmable wires
Specialized wiring structure for all routes

Field Programmable Gate Array - FPGA




COE COLLEGE®

How programming has changed overtime

In early days (10-32 flip-flops):

I draw this:

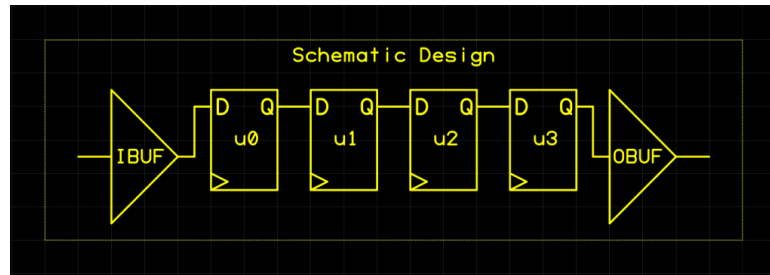


Software (EDA) will do this (a netlist):

```
...
(cell top_shift_register (cellType GENERIC)
(interface
(port (identifier SI) (direction INPUT))
(port (identifier CLK) (direction INPUT))
(port (identifier RST) (direction INPUT))
(port (identifier Q0) (direction OUTPUT))
(port (identifier Q1) (direction OUTPUT))
(port (identifier Q2) (direction OUTPUT))
(port (identifier Q3) (direction OUTPUT))
)
(contents
(instance i_dff0 (view netlist) (cell DFF) (library generic_gates))
(instance i_dff1 (view netlist) (cell DFF) (library generic_gates))
(instance i_dff2 (view netlist) (cell DFF) (library generic_gates))
(instance i_dff3 (view netlist) (cell DFF) (library generic_gates))
)
)
...
```

Later I use Verilog:

```
1 `timescale 1 ns/ 100 ps
2 `default_nettype none // Strictly enforce all nets to be declared
3
4 module top
5 (
6   input wire      clk,
7   output wire [3:0] led
8 ); // module top
9
10  wire clk_100m_loc;
11  wire clk_100m_tree;
12  wire u0_q;
13  wire u1_q;
14  wire u2_q;
15  wire u3_q;
16
17  IBUF i0 ( .I( clk ), .O( clk_100m_loc ) );
18  OBUF i1 ( .I( clk_100m_loc ), .O( clk_100m_tree ) );
19
20  FDSE u0 ( .S(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u3_q ), .Q( u0_q ) );
21  FDRE u1 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u0_q ), .Q( u1_q ) );
22  FDRE u2 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u1_q ), .Q( u2_q ) );
23  FDRE u3 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u2_q ), .Q( u3_q ) );
24
25  OBUF j0 ( .I( u0_q ), .O( led[0] ) );
26  OBUF j1 ( .I( u1_q ), .O( led[1] ) );
27  OBUF j2 ( .I( u2_q ), .O( led[2] ) );
28  OBUF j3 ( .I( u3_q ), .O( led[3] ) );
29
30 endmodule // top.v
31 `default_nettype wire // enable Verilog default for any 3rd party IP needing it
```

Then I use this design codes to “build”:

 

COE COLLEGE

How programming has changed overtime

Verilog

```
19
20  FDSE u0 ( .S(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u3_q ), .Q( u0_q ) );
21  FDRE u1 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u0_q ), .Q( u1_q ) );
22  FDRE u2 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u1_q ), .Q( u2_q ) );
23  FDRE u3 ( .R(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u2_q ), .Q( u3_q ) );
24
```

With higher level language, the codes are now more readable:

```
FDSE u0 ( .S(0), .CE(pulse_1hz), .C( clk_100m_tree ), .D( u3_q ), .Q( u0_q ) );

always @ ( posedge clk_100m_tree ) begin
    if ( pulse_1hz == 1 ) begin
        u0_q <= u3_q;
    end
end
```

Higher language options:

System Verilog (RTL Verilog)

SystemVerilog

```
module inv(input  logic [3:0] a,
           output logic [3:0] y);

    assign y=~a;
endmodule
```

a[3:0] represents a 4-bit bus. The bits, from most significant to least significant, are a[3], a[2], a[1], and a[0]. This is called *little-endian* order, because the least significant bit has the smallest bit number. We could have named the bus a[4:1], in which case a[4] would have been the most significant. Or we could have used a[0:3], in which case the bits, from most significant to least significant, would be a[0], a[1], a[2], and a[3]. This is called *big-endian* order.

VHDL

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity inv is
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of inv is
begin
    y <= not a;
end;
```

VHDL uses STD_LOGIC_VECTOR to indicate busses of STD_LOGIC. STD_LOGIC_VECTOR(3 downto 0) represents a 4-bit bus. The bits, from most significant to least significant, are a(3), a(2), a(1), and a(0). This is called *little-endian* order, because the least significant bit has the smallest bit number. We could have declared the bus to be STD_LOGIC_VECTOR(4 downto 1), in which case bit 4 would have been the most significant. Or we could have written STD_LOGIC_VECTOR(0 to 3), in which case the bits, from most significant to least significant, would be a(0), a(1), a(2), and a(3). This is called *big-endian* order.

 


Figure 4.3 inv synthesized circuit

Higher language options:

System Verilog (RTL Verilog)

SystemVerilog

```
module inv(input  logic [3:0] a,
           output logic [3:0] y);

    assign y=~a;
endmodule
```

a[3:0] represents a 4-bit bus. The bits, from most significant to least significant, are a[3], a[2], a[1], and a[0]. This is called *little-endian* order, because the least significant bit has the smallest bit number. We could have named the bus a[4:1], in which case a[4] would have been the most significant. Or we could have used a[0:3], in which case the bits, from most significant to least significant, would be a[0], a[1], a[2], and a[3]. This is called *big-endian* order.

VHDL

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity inv is
    port(a: in  STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of inv is
begin
    y <= not a;
end;
```

VHDL uses STD_LOGIC_VECTOR to indicate busses of STD_LOGIC. STD_LOGIC_VECTOR(3 downto 0) represents a 4-bit bus. The bits, from most significant to least significant, are a(3), a(2), a(1), and a(0). This is called *little-endian* order, because the least significant bit has the smallest bit number. We could have declared the bus to be STD_LOGIC_VECTOR(4 downto 1), in which case bit 4 would have been the most significant. Or we could have written STD_LOGIC_VECTOR(0 to 3), in which case the bits, from most significant to least significant, would be a(0), a(1), a(2), and a(3). This is called *big-endian* order.

 


Figure 4.3 inv synthesized circuit

More HDL examples:

HDL Example 4.4 EIGHT-INPUT AND

SystemVerilog

```
module and8(input  logic [7:0] a,
            output logic      y);

    assign y = &a;

    // &a is much easier to write than
    // assign y = a[7] & a[6] & a[5] & a[4] &
    //           a[3] & a[2] & a[1] & a[0];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity and8 is
    port(a: in  STD_LOGIC_VECTOR(7 downto 0);
         y: out STD_LOGIC);
end;

architecture synth of and8 is
begin
    y <= and a;
    -- and a is much easier to write than
    -- y <= a(7) and a(6) and a(5) and a(4) and
    --       a(3) and a(2) and a(1) and a(0);
end;
```

 


Figure 4.5 and8 synthesized circuit



More HDL examples:

HDL Example 4.5 2:1 MULTIPLEXER

SystemVerilog

The *conditional operator* `?:` chooses, based on a first expression, between a second and third expression. The first expression is called the *condition*. If the condition is 1, the operator chooses the second expression. If the condition is 0, the operator chooses the third expression.

`?:` is especially useful for describing a multiplexer because, based on the first input, it selects between two others. The following code demonstrates the idiom for a 2:1 multiplexer with 4-bit inputs and outputs using the conditional operator.

```
module mux2(input  logic [3:0] d0, d1,
            input  logic      s,
            output logic [3:0] y);

    assign y = s ? d1 : d0;
endmodule
```

If `s` is 1, then `y = d1`. If `s` is 0, then `y = d0`.

`?:` is also called a *ternary operator*, because it takes three inputs. It is used for the same purpose in the C and Java programming languages.

VHDL

Conditional signal assignments perform different operations depending on some condition. They are especially useful for describing a multiplexer. For example, a 2:1 multiplexer can use conditional signal assignment to select one of two 4-bit inputs.

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux2 is
    port(d0, d1: in  STD_LOGIC_VECTOR(3 downto 0);
         s:      in  STD_LOGIC;
         y:      out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of mux2 is
begin
    y <= d1 when s else d0;
end;
```

The conditional signal assignment sets `y` to `d1` if `s` is 1. Otherwise it sets `y` to `d0`. Note that prior to the 2008 revision of VHDL, one had to write `when s = '1'` rather than `when s`.

 


Figure 4.6 mux2 synthesized circuit

More modern FPGA dev:

<https://www.pynq.io/>



[Home](#) [Get Started](#) [Boards](#) [Community](#) [Source Code](#) [Support](#)


What is PYNQ?

PYNQ™ is an open-source project from AMD® that makes it easier to use Adaptive Computing platforms.

Using the Python language, Jupyter notebooks, and the huge ecosystem of Python libraries, designers can exploit the benefits of programmable logic and microprocessors to build more capable and exciting electronic systems.

PYNQ can be used to create high performance applications with:

 - parallel hardware execution
- high frame-rate video processing
- hardware accelerated algorithms
- real-time signal processing
- high bandwidth IO
- low latency control



https://github.com/Xilinx/PYNQ_Workshop