

# **ENR-325/325L Principles of Digital Electronics and Laboratory**

Xiang Li  
Fall 2025

# Hamming codes can be done in the EE way

- Before that, we need to acquire some basic skillsets.

Pre-step: Data forms

Step 1: Data manipulation

Step 2: Information storage


**Step 3: Interface**

**3.1 Information flow**

~~3.2 Physical contacts~~ (better stuff to talk about in PCB designs)

# Understanding SR latch with truth table and timing diagram


SR latch

 


SR latch truth table

S	R	Output (Q)
0	0	Previous State (HOLD)
0	1	0
1	0	1
1	1	0 (Invalid)

SR Latch Timing Diagram (NOR Gates)

 


# A latch with a “single” input

 

[https://en.wikipedia.org/wiki/Flip-flop\\_\(electronics\)](https://en.wikipedia.org/wiki/Flip-flop_(electronics))

A gated D latch

 


D latch truth table


D	E	Output (Q)
X	0	<b>Previous State</b>
0	1	<b>0</b>
1	1	<b>1</b>

# A latch with a “single” input


A gated D latch

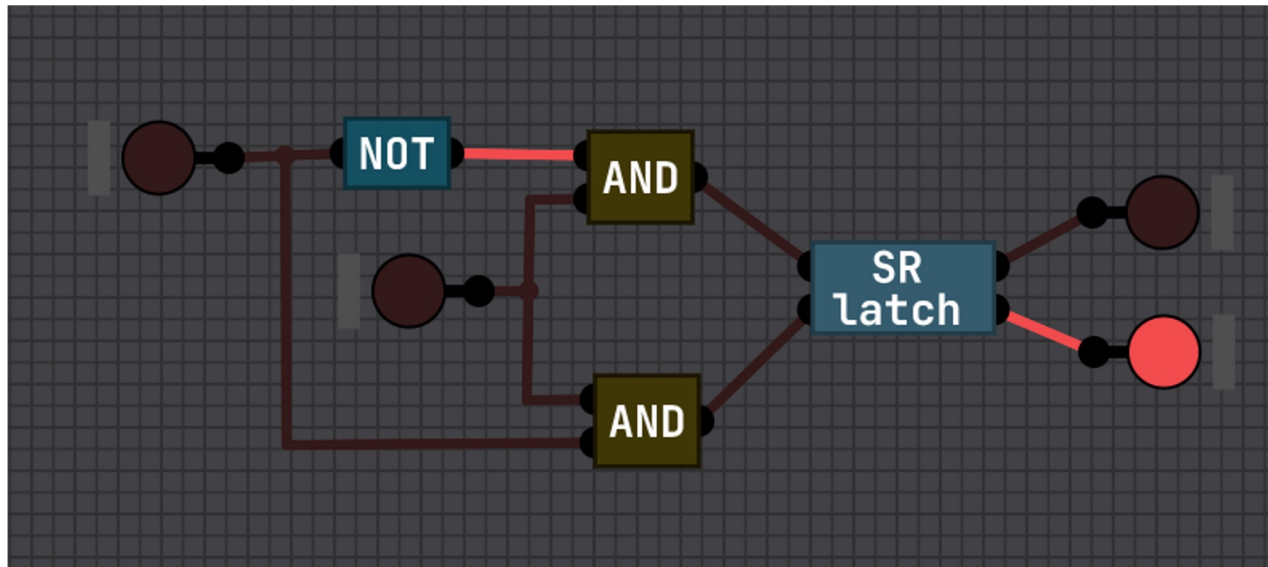




Also known as: D latch/data latch

 


Gated D latch

 


# A clocked D latch

   


# Timing diagram code:

 
 
```
1 {  
2   "signal": [  
3     {"name": "CLK",      "wave": "lhlhlhl"},  
4     {"name": "D",        "wave": "lpphppl"},  
5     {"name": "Q",        "wave": "lp lh.pl"},  
6   ],  
7   "head": {  
8     "text": "Clocked gated D latch)"  
9   },  
10  "config": {  
11    "hscale": 2  
12  }  
13 }  
14 }  
15 }  
16 }
```



 
# Rising edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:  
Master-slave D type flip flop


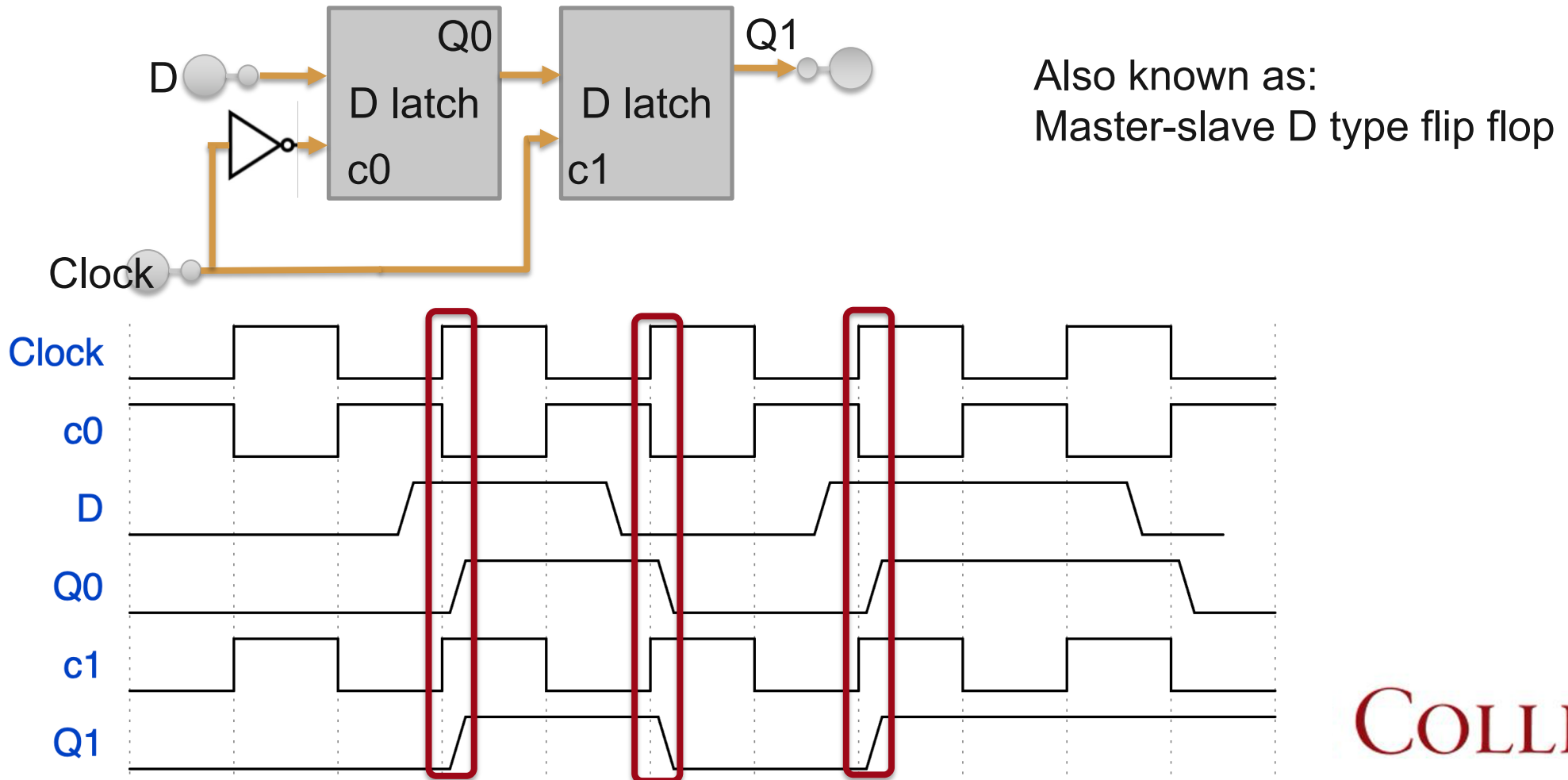
# Rising edge-triggered flip flops: synchronizing (timed trigger) achieved



 
# Falling edge-triggered flip flops: synchronizing (timed trigger) achieved




Also known as:  
Master-slave D type flip flop

Timing diagram is in HW#7.

# One more application with D flip-flops

 


# So, this is a (4 bit) shift register

 

- **Serial In (SI), Serial Out (SO)**
- **How about SIPO, PISO, and PIPO?**
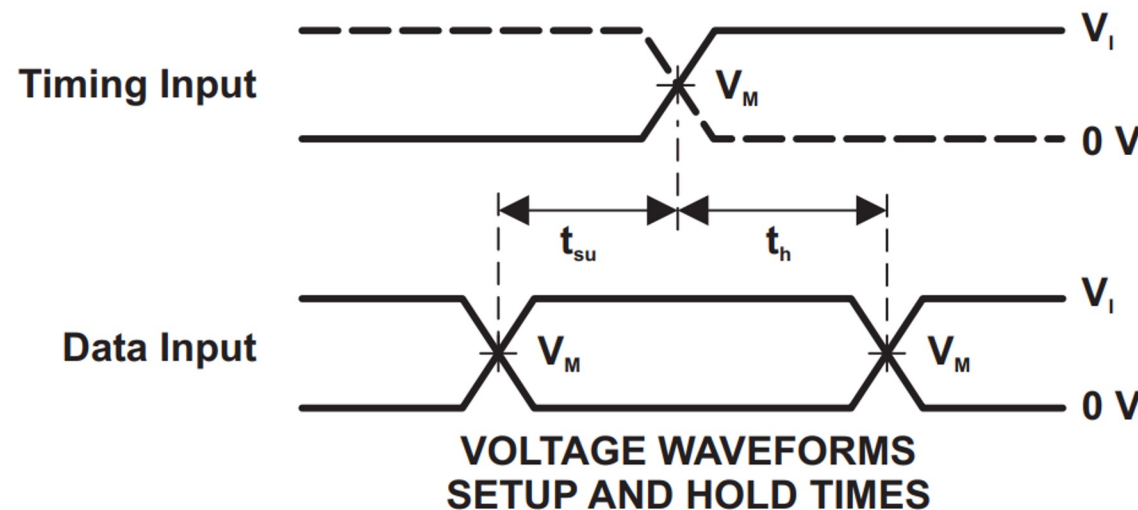
# Dynamic discipline: handling the interface between logics and time

- A clock signal (with its edges if it's a flip-flop) to define transitions.
- Stable inputs during that transition window. (So, some *setup time*  $t_{su}$  and some *hold time*  $t_h$ )
- Thus, guaranteed viable output other than its own switching delays.






COE COLLEGE®

# Dynamic discipline: handling the interface between logics and time

- Unlike propagation delay ( $t_{pd}$ ) and contamination delay ( $t_{cd}$ ), the setup time  $t_{su}$  and some hold time  $t_h$  are intentional.
- So, the final time constraint for sequential logics is:

Minimum clock period:  $T_c \geq \Sigma t_{pd} + t_{su}$

   Minimum delay constraint:  $\Sigma t_{cd} \geq t_h$



COE COLLEGE®

# Dynamic discipline:

Timing Requirements (Over Recommended Operating Free-air Temperature Range (unless otherwise noted)) (see Figure 2)

			SN54LVTH16646				SN74LVTH16646				UNIT
			$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		$V_{CC} = 3.3\text{ V}$ $\pm 0.3\text{ V}$		$V_{CC} = 2.7\text{ V}$		
			MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
$f_{\text{clock}}$	Clock frequency		150		150		150		150		MHz
$t_w$	Pulse duration, CLK high or low		3.3		3.3		3.3		3.3		ns
$t_{\text{su}}$	Setup time, A or B before CLKAB↑ or CLKBA↑	Data high	1.2		1.5		1.2		1.5		ns
		Data low	2		2.8		2		2.8		
$t_h$	Hold time, A or B after CLKAB↑ or CLKBA↑	Data high	0.5		0		0.5		0		ns
		Data low	0.5		0.5		0.5		0.5		

Figure 14. Example Timing-Requirements Section